

2 АУДИТОРНЕ ВЈЕЖБЕ


3 АУДИТОРНЕ ВЈЕЖБЕ (С ТИМ ДА НИЈЕ ПОТРЕБНО НИКАКВО ПРИЛАГОЂЕЊЕ)

1.

$$V_o = \frac{R_2}{R_1 + R_2} V_i \Rightarrow V_i = \frac{R_1 + R_2}{R_2} \cdot V_o$$

за  $V_i > \frac{R_1 + R_2}{R_2} \cdot V_o$  :  $D$  баци,  $I_{R_1} = \frac{V_i - V_D}{R_1}$ ,  $I_D = \frac{V_i - V_D}{R_1} - \frac{V_D}{R_2}$

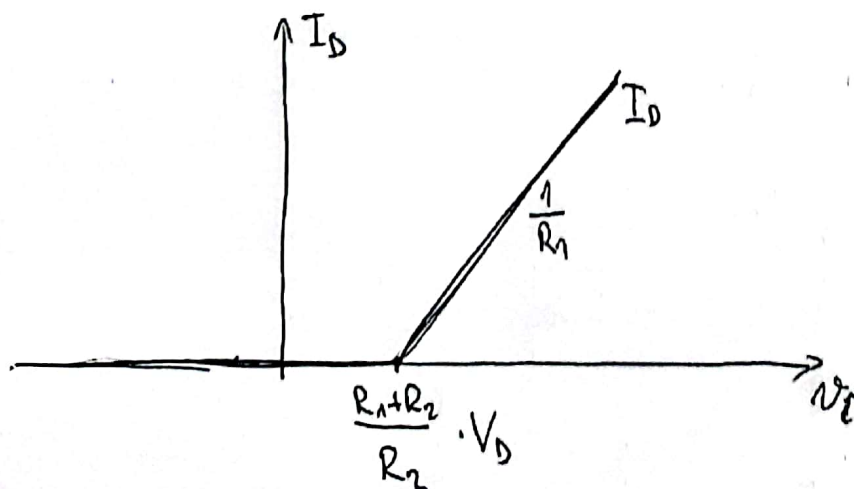за  $V_i < \frac{R_1 + R_2}{R_2} \cdot V_o$  :  $D$  не баци,  $I_{R_1} = \frac{V_i}{R_1 + R_2}$ ,  $I_D = 0$



4

A	B	Y
0	0	1
0	1	1
1	0	0
1	1	0

$$Y = \overline{A}$$

КОГДА ЧА  $T_2$  НЕ УТИЧЕ НА  $Y$ .

$A=0 \Rightarrow D_1$  ON  $D_2$  OFF  $Q_1$  HE BOAL

$A=1 \Rightarrow D_1$  OFF  $D_2$  ON  $Q_1$  BOAL

$$I_{CS} = \frac{V_{CC} - V_{CES}}{R_C}$$

$$I_{BS} = \frac{I_{CS}}{\beta_{min}} = \frac{V_{CC} - V_{CES}}{\beta_{min} R_C}$$

$$I_B = \frac{V_{CC} - V_D - V_{BES}}{R_1}$$

$$F_S = \frac{I_B}{I_{BS}} \Rightarrow I_B = 3 I_{BS}$$

$$\frac{V_{CC} - V_D - V_{BES}}{R_1} = \frac{3(V_{CC} - V_{CES})}{\beta_{min} R_C}$$

$$R_C = \frac{3 R_1 (V_{CC} - V_{CES})}{\beta_{min} (V_{CC} - V_D - V_{BES})}$$

$$= 960 \Omega$$