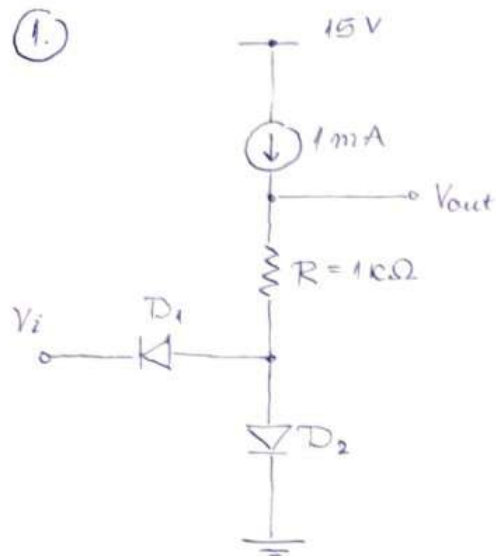


Основи електроніки та гн'ячальні техніки

РІШЕННЯ

1.



1° $V_i < 0V$

Кожа D_1 провони, D_2 не провони


$$V_{out} = V_{in} + 1V$$

2° $V_i > 0V$

Кожа D_2 провони, D_1 не провони


$$V_{out} = 1mA \cdot R$$

$$V_{out} = 1V$$

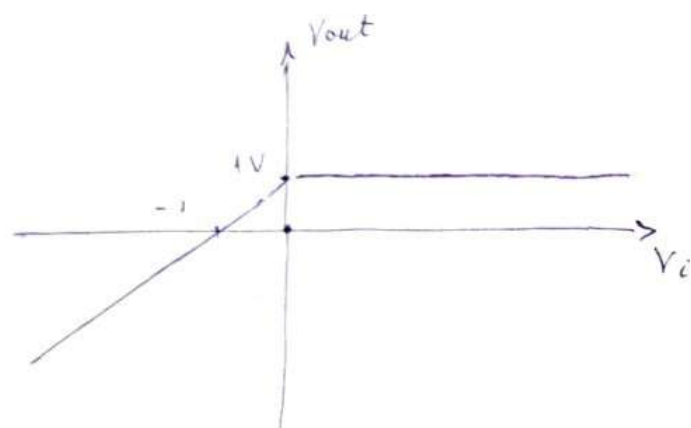


1° $V_{out} = 0 \Rightarrow V_{in} = -1V \quad (-1, 0)$

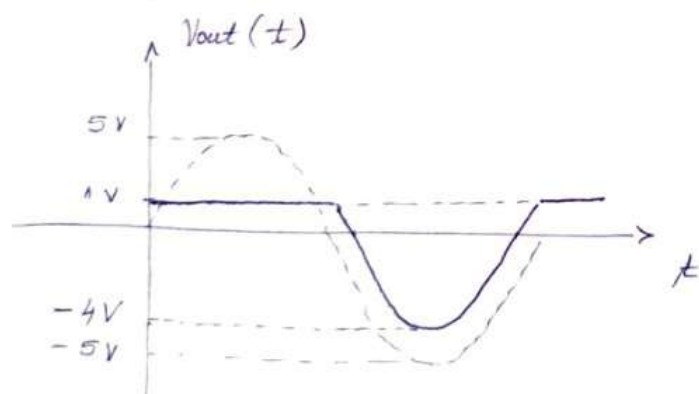$V_{in} = 0 \Rightarrow V_{out} = 1V \quad (0, 1)$



(2.)

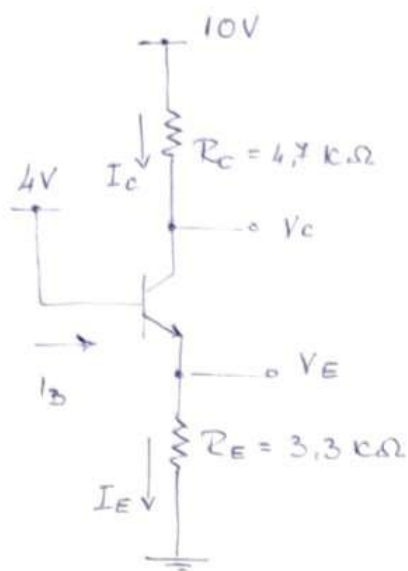

Претпоставимо активни режим.

$$V_E = V_B - V_{BE}$$

$$V_E = 4V - 0.7V$$

$$V_E = 3.3V$$

$$I_E = \frac{V_E}{R_E} = 1mA$$

$$I_C = \alpha I_E, \quad \alpha = \frac{\beta}{1+\beta} \approx 0.99$$

$$I_C = 0.99mA$$

$$V_C = 10V - R_C I_C$$

$$V_C = 10V - 0.99mA \cdot 4.7k\Omega$$

$$V_C \approx 5.3V$$

$$V_{BC} = V_B - V_C$$


$$V_{BC} = 4V - 5.3V$$

$$V_{BC} = -1.3V$$

Претпоставка је добра!

$$I_B = \frac{I_E}{1+\beta} = 0.01mA$$

(3.)

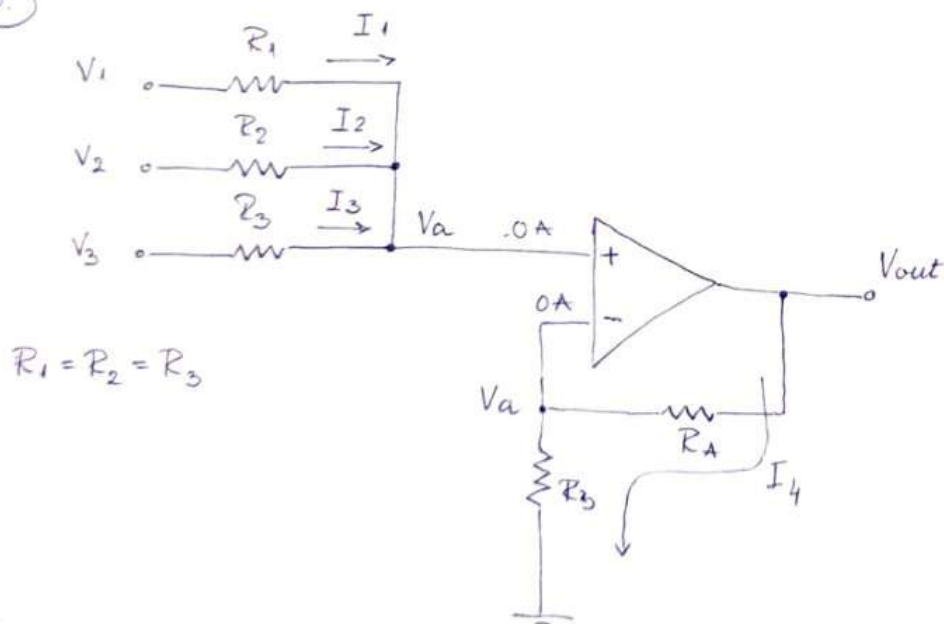

$$R_1 = R_2 = R_3$$

$$I_1 + I_2 + I_3 = 0$$

$$\frac{V_1 - V_a}{R_1} + \frac{V_2 - V_a}{R_2} + \frac{V_3 - V_a}{R_3} = 0$$

$$I_4 = \frac{V_a}{R_B}, \quad I_4 = \frac{V_{out} - V_a}{R_A}$$

$$\frac{V_a}{R_B} = \frac{V_{out} - V_a}{R_A}$$

$$V_a = V_{out} \frac{R_B}{R_B + R_A}$$


$$V_1 - V_a + V_2 - V_a + V_3 - V_a = 0$$

$$V_1 + V_2 + V_3 = 3V_a$$


$$3 \cdot V_{out} \frac{R_B}{R_B + R_A} = V_1 + V_2 + V_3 \Rightarrow V_{out} = \frac{1}{3} \left(1 + \frac{R_A}{R_B} \right) (V_1 + V_2 + V_3)$$

$$A = \frac{1}{3} \left(1 + \frac{R_A}{R_B} \right)$$

(1.)

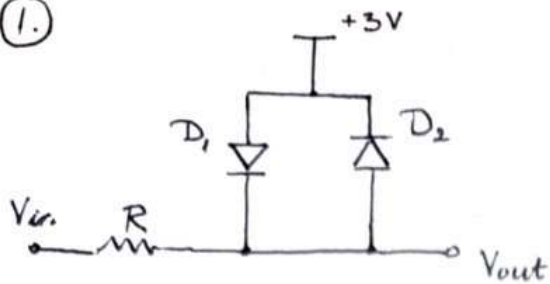

1° D_1 богу, D_2 не богу

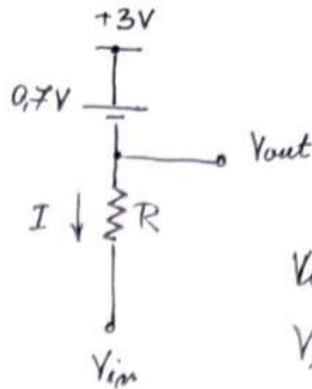

$$R = 500 \Omega$$

$$I = 1 \text{ mA}$$

~~$V_{out} = V_{in} + RI$~~

$$V_{in} + RI - V_{out} = 0$$

$$V_{out} = V_{in} + RI$$

$$V_{out} + 0.7V - 3V = 0$$

$$V_{out} = 2.3V$$

$$V_{in} = V_{out} - RI$$


$$V_{in} = V_{out} - RI$$

$$V_{in} = 2.3V - 500 \cdot 1 \text{ mA}$$

$$V_{in} = 2.3V - 0.5V$$

$$V_{in} = 1.8V$$

2° D_1 не богу, D_2 богу

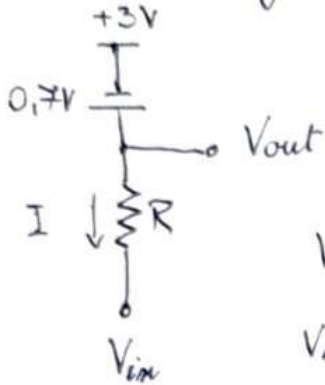

$$V_{out} - 0.7V - 3V = 0$$

$$V_{out} = 3.7V$$

$$V_{out} = V_{in} + RI$$


$$V_{in} = V_{out} - RI$$

$$V_{in} = 3.7V - 500 \cdot 1 \text{ mA}$$


$$V_{in} = 3.7V - 0.5V$$

$$V_{in} = 3.2V$$

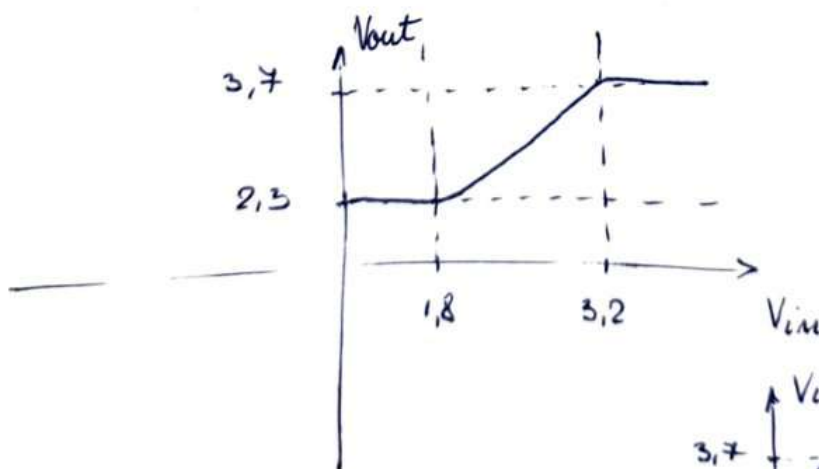
$$V_{out} = \begin{cases} 2.3V, & V_{in} \leq 1.8V \\ V_{in}, & 1.8 < V_{in} < 3.2V \\ 3.7V, & V_{in} \geq 3.2V \end{cases}$$



ПРЕХОДА
ХАРАКТЕРИСТИКА

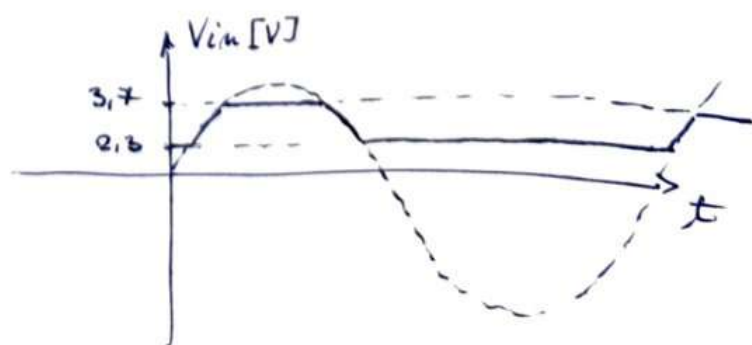

(2.)

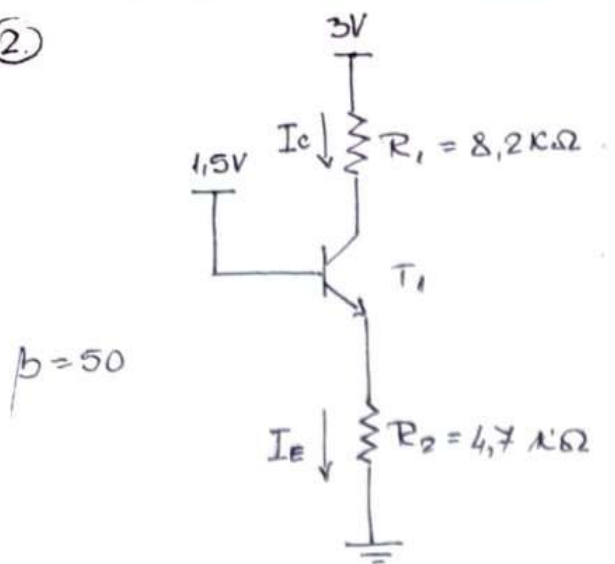

$$V_C = 3V - R_C I_C$$

$$V_C = 3V - 8.2k \cdot 0.16mA$$

$$V_C = 3V - 1.4V$$

$$V_C \approx 1.6V$$

$$I_B = \frac{I_C}{\beta} = \frac{0.16mA}{50} = 0.0032mA$$

$$V_{BC} = V_B - V_C = 1.5V - 1.6V = -0.1V$$

Како је ~~у~~ $V_{BC} < 0$, из пријетоставку да је $V_{BE} = 0.7V$, знам да смо у активном режиму и пријетоставка је добра.

Пријетоставимо активни режим.

$$V_{BE} = 0.7V, V_{BE} = V_B - V_E$$

$$V_E = V_B - V_{BE}$$

$$V_E = 1.5V - 0.7V$$

$$V_E = 0.8V$$


$$I_E = \frac{V_E - 0V}{R_2} = \frac{0.8V}{4.7k\Omega} = 0.17mA$$

$$I_C = \alpha I_E, \alpha = \frac{\beta}{1 + \beta}$$

$$I_C = \frac{50}{51} I_E = 0.98 \cdot 0.17mA$$

$$I_C = 0.16mA$$

3.

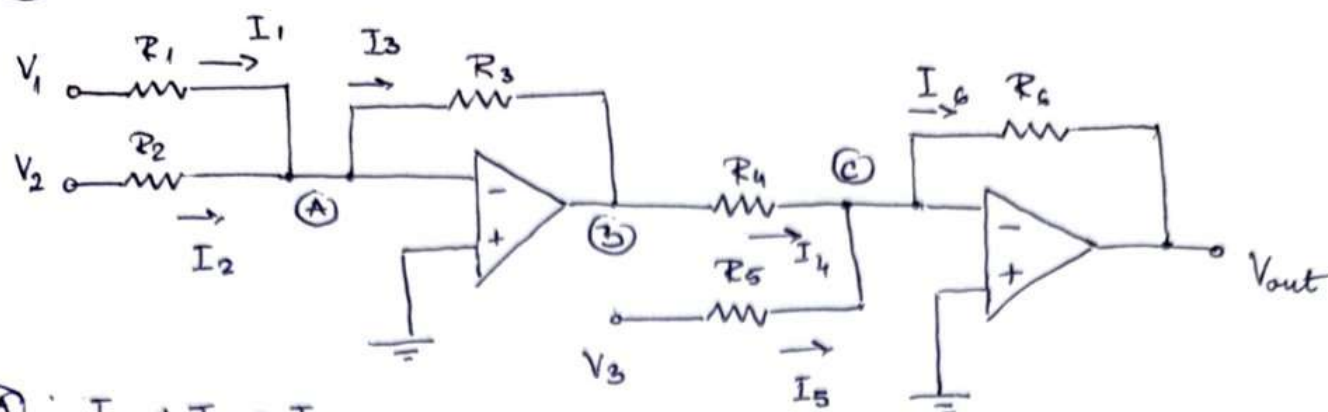

(A) : $I_1 + I_2 = I_3$

$$\frac{V_1 - V_a}{R_1} + \frac{V_2 - V_a}{R_2} = \frac{V_a - V_b}{R_3} \quad / \cdot R_1 R_2 R_3$$

$$R_2 R_3 V_1 - \cancel{R_2 R_3 V_a} + R_1 R_3 V_2 - \cancel{R_1 R_3 V_a} = \cancel{R_1 R_2 V_a} - R_1 R_2 V_b$$

$V_a = 0V$ због вкупногено масе

$$R_2 R_3 V_1 + R_1 R_3 V_2 = -R_1 R_2 V_b \quad / : R_1 R_2$$

$$V_b = - \left(V_1 \frac{R_3}{R_1} + V_2 \frac{R_3}{R_2} \right) \quad (1)$$

(C) : $I_4 + I_5 = I_6$

$$\frac{V_b - V_c}{R_4} + \frac{V_3 - V_c}{R_5} = \frac{V_c - V_{out}}{R_6}, \quad V_c \text{ je masota vupnyennna masa na je } V_c = 0V$$

$$\frac{V_b}{R_4} + \frac{V_3}{R_5} = - \frac{V_{out}}{R_6} \quad / \cdot R_6$$

$$V_{out} = - \left(\frac{R_6}{R_4} V_b + \frac{R_6}{R_5} V_3 \right), \text{ uvvrshabamo (1)}$$

$$V_{out} = - \left(-V_1 \frac{R_3 R_6}{R_1 R_4} - V_2 \frac{R_3 R_6}{R_2 R_4} + \frac{R_6}{R_5} V_3 \right)$$

$$V_{out} = V_1 \frac{R_3 R_6}{R_1 R_4} + V_2 \frac{R_3 R_6}{R_2 R_4} - \frac{R_6}{R_5} V_3$$

Како мна улогу тежинокој садирага.